

# Lab #4: Sequential Logic Design Using Schematics


## Introduction

In the previous lab you built combinational logic circuits where the output was an instantaneous function that depended on the current input only. In this lab you will build **sequential logic** circuits where the outputs depend on the current and *previous history* of outputs, and generally change only when 'clocked' by a clock signal. The **memory** components within the sequential logic are what allows for the dependence on *previous history*. A 1-bit memory device is known as a **flip-flop** (FF) or a **latch**.

- In part 4.1 you will design a **Set-Reset flip-flop (SRFF)**, with additional **Preset** and **Clear** inputs (which are useful to force the initial output to be a **1** (Preset) or **0** (clear), respectively).
- In part 4.2 you use three **D flip-flops (DFFs)** from the Component Library browser to design a **Counter** circuit which counts or steps to the next value in a sequence of numbers on each clock pulse.
- In part 4.3 you will use two **D flip-flops** to design a **Finite State Machine** circuit.
- You will manually assign pins to your input/output signals.
- Read through the entire part before starting!

## 4.1 Set-Reset Flip-flop (SRFF) Design and Implementation

 1. A circuit for an SR flip-flop is shown here: →
  - **Cp** is the clock pulse input
  - The inputs **M** and **N** are signals that can be used to **Preset** or **Clear** the output **asynchronously** (i.e. without waiting for a clock pulse), but your cruel professor has not told you which is which!
  - Assuming the clock pulse is *inactive*, derive the truth table from the circuit diagram: →
    - Hence determine which of the two inputs, **M** and **N** is the **Preset** input (sets **y** to 1): \_\_\_\_\_  
is the **Clear** input (sets **y** to 0): \_\_\_\_\_
    - Also determine whether the M, N are **active low** or **active high** signals: \_\_\_\_\_
2. When M & N are inactive, SRFF functions as follows
  - **S** sets the output **y** to **1** on the next **clock edge**
  - **R** resets the output **y** to **0** on the next **clock edge**
  - **y** stays the same value when SR are set to 00
  - **y'** is always the opposite of the output **y** when



M	N	$y^+$	$y'^+$
0	0		
0	1		
1	0		
1	1		

**Note:** M and N should be used only for forcing the initial state, and should be held **inactive** most of the time, since they override the regular SR behavior.

3. Implement your SRFF design within Quartus:

- Create a new Project called **Lab4P1**, and within it a **File>New>Schematic** diagram called **SRflipFlop.bdf**. Create the SRFF diagram on Page 1 in this schematic. Add an **inverter** to the clock signal Cp (because the push-buttons go low when pressed and you want the clock to go high when pressed). Set SRflipflop.bdf as the top design. Compile.
- **Assign pins:** In the past, you have been importing pin assignments from a given file. Starting this lab, you will assign pins to your input/output signals using **Pin Planner**. A **pin assignment table of the DE10 board** is posted in the Lab Assignments folder.
  - Click **Assignments> Pin Planner**. Adjust the window boundaries to see the table listing the inputs/outputs of your design. Adjust the columns so you can see the full pin names. Pin Assignments will be placed in the Location column.
  - Open the **DE10 pin assignment table** in BB.
  - For each of the signals below, click in the **Location** cell to select the pin name you want to connect to (check the pin table) and choose “3.3-V LVTTTL” in the **I/O standard** column.
    - Assign **Cp** to the pin of **KEY[0]**
    - Assign the pins of **SW[3]..SW[0]** to the **S**, **R**, **M**, and **N** inputs, respectively.
    - Assign the pins of **LEDR[1]** and **LEDR[0]** to the **y** and **y'** outputs, respectively.
  - Compile (compile is needed every time you make change to your project).

4. Compile, Program, and **test** your circuit on the **DE10** board.

**Demonstrate the following to the instructor/TA:**

- Show you have completed the analysis in section 4.1.2
- With the **clock** input *inactive*, demonstrate that the **M** and **N** inputs work correctly.
- With **M** and **N** *inactive*, demonstrate that the **S** and **R** inputs work correctly along with the **clock**.

## 4.2 Counter Design and Implementation

In this part, you will design a counter and implement it using Quartus. You can obtain your personalized counter specification from the instructor/TA.

1. Design the circuit using **three** D flip-flops and whatever other gates required. The circuit must be *minimized; i.e., it should use the minimum number of logic gates possible*.
  - Make a **Next State** table for your counter, including unused states.
  - Create a **Karnaugh map** for each D input of your counter, and from them derive minimized expressions for the excitation functions **D2..D0**.
  - Also predict the next state when the counter is set to one of the **unused states**.
  - Sketch the circuit you will build to implement your counter with **three** DFFs.
  - Take a picture of your counter page with your work and keep it in your 4.2 folder.
  - You will also need your counter design in Lab 5. So keep it (and your specification sheet)!

**Have your circuit checked by the instructor/TA before proceeding further.**

2. Implement your circuit in Quartus:

- Create a new Project called **Lab4P2**, and within it a **File>New>Schematic** diagram called **Counter.bdf**. Recreate your counter circuit in this schematic.
  - Use **Primitives>Storage>DFF** (D-type Flip-Flop) from the Component Library browser for your flip flops.
  - Add an inverter to the clock signal of the DFFs. Compile.
- Assign pins in **Pin Planner**:
  - Connect the Preset (**PREN**) signals of your three DFFs to switches **SW[9]** to **SW[7]**, respectively. Note: these signals are active low.
  - Connect the Clear (**CLRN**) signals of your three DFFs to switches **SW[6]** to **SW[4]**, respectively. Note: these signals are active low.
  - Connect the counter output (the outputs of your three flip-flops) to **LEDR[2]..LEDR[0]**, respectively.
  - Connect **Key[0]** to the **clock** signal.

3. Compile, Program and **test** your circuit on the **DE10** board. Test the preset and clear (reset) signals first, then make them inactive when testing the counter circuit.

**Demonstrate the following to the instructor/TA:**

- When PRENs and CLRNs are set inactive, the main counting **sequence**/cycle is generated correctly as you clock your circuit
- Force the circuit into each of the three **unused** states (using the corresponding Clear and Preset inputs) and verify your predictions of unused states.

## 4.3 Finite State Machine Design and Implementation

In this part, you will design a finite state machine and implement it using Quartus. You can obtain your personalized **state machine** specification from the instructor/TA.

1. Design the circuit using **two** D flip-flops and whatever other gates are required.

- **Substitute** state variable values into the next state table and **rearrange** the rows into Karnaugh map form.
- Hence create a **Karnaugh** map for each state bit **Q1..Q0** and input of your state machine and from them derive minimized expressions for the excitation functions **D1, D0**, and for the output function **z**.
- **Sketch** the circuit you will build to implement your machine with the **two** flip-flops.
- Take a picture of your counter page with your work and keep it in your 4.3 folder.
- You will also need your state machine design in Lab 5. So keep it (**and your specification sheet**)!

**Have your circuit checked by the instructor/TA before proceeding further.**

2. Implement your circuit in Quartus:

- Create a new Project called **Lab4P3**, and within it a **File>New>Schematic** diagram called **FSM.bdf**. Recreate your state machine circuit in this schematic.
- Assign pins in **Pin Planner**
  - Connect the FSM states **Q1..Q0** to **LEDR[1]..LEDR[0]**, respectively, and the output **z** to **LEDR[2]**.
  - Connect your input **x** to **SW[0]**, and the Preset (**PREN**) and Clear (**CLRN**) signals of your two DFFs to switches **SW[5]** and **SW[4]**, respectively. Note: these signals are active low.
  - Feed input **Key[0]** through an **inverter** and then use this to **clock** your flip-flops.
- Compile, Program and **test** your circuit on the **DE10** board.

**Demonstrate the following to the instructor/TA:**

- Force the circuit into state A using the preset/clear inputs. Then demonstrate that you can step through all states of the **next state table** in your original state machine assignment paper.

**Submission for Lab 4:**

After you have been checked off all the parts by the instructor/TA, zip all the Lab4 project folders into one zip file, name the zip file Lab4\_<your last name>.zip, and submit it to Lab assignment in Blackboard. Please only submit one submission to blackboard, and please ensure everything is contained in the single zip file.